

O.P.Code: 25EE2103

R25

H.T.No.

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

M.Tech I Year I Semester Regular Examinations January-2026

DC DRIVES

(Power Electronics)

Time: 3 Hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

1 Explain the operation of a single-phase semi-converter feeding a DC motor load with neat diagrams. CO1 L2 12M

OR

2 Compare the performance of semi-converter and full-converter drives under continuous and discontinuous conduction modes. CO1 L4 12M

UNIT-II

3 Explain the operation of a three-phase bridge rectifier with resistive load using circuit diagram and waveforms. CO2 L2 12M

OR

4 Explain how a three-phase converter operates as an inverter with appropriate gating sequence. CO2 L3 12M

UNIT-III

5 Derive the transfer function of a converter-fed DC motor drive system. CO3 L3 12M

OR

6 Describe the control circuit of a three-phase converter drive with a neat block diagram. CO3 L2 12M

UNIT-IV

7 Describe the working of a closed-loop speed control system for a DC motor using block diagram. CO4 L2 12M

OR

8 Derive the dynamic model equations of a current-controlled DC motor drive. CO4 L4 12M

UNIT-V

9 Define four-quadrant operation of a chopper-fed DC drive with neat waveforms. CO5 L2 12M

OR

10 Derive the expression for average armature voltage and current in a chopper-fed DC motor. CO6 L3 12M

*** END ***