

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B.Tech. II Year II Semester Regular Examinations July/August-2025

ELECTRONIC CIRCUITS ANALYSIS
(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions **10 x 2 = 20 Marks**)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | What is the need for multistage amplifiers? | CO1 | L1 | 2M |
| | b | What is a Differential amplifier? | CO2 | L2 | 2M |
| | c | List the internal capacitances of BJT differential amplifier. | CO1 | L1 | 2M |
| | d | Define f_T and f_{β} . | CO1 | L1 | 2M |
| | e | List the four basic feedback topologies. | CO1 | L2 | 2M |
| | f | Explain Barkhausen criterion. | CO1 | L2 | 2M |
| | g | Define Power amplifier. List the different types of power amplifiers. | CO3 | L1 | 2M |
| | h | What are the advantages of power MOSFETs over power BJTs? | CO3 | L1 | 2M |
| | i | A tuned amplifier has a resonant frequency of 1 MHz and bandwidth of 10 kHz. Calculate the Quality Factor (Q) of the amplifier. | CO2 | L4 | 2M |
| | j | Define Multivibrator and mention its applications. | CO2 | L1 | 2M |

PART-B

(Answer all Five Units **5 x 10 = 50 Marks**)

UNIT-I

- | | | | | | |
|-----------|---|---|-----|----|----|
| 2 | a | Discuss various coupling schemes used in multistage amplifiers. | CO2 | L2 | 5M |
| | b | Explain the operation of RC coupled amplifier with frequency response curve. | CO1 | L2 | 5M |
| OR | | | | | |
| 3 | a | Construct the basic structure of MOS and BJT differential amplifiers. | CO1 | L2 | 5M |
| | b | Analyze BJT differential amplifier with a neat circuit diagram for common mode operation. | CO2 | L3 | 5M |

UNIT-II

- | | | | | | |
|-----------|---|--|-----|----|----|
| 4 | a | Derive the break frequencies of CS (Common Source) amplifier at low frequencies. Obtain the expression for overall gain or transfer function and draw the frequency response | CO2 | L3 | 8M |
| | b | Draw the high frequency model of MOSFET. | CO1 | L1 | 2M |
| OR | | | | | |
| 5 | a | With relevant circuit diagrams, explain the internal capacitive effects of MOSFET. | CO2 | L2 | 5M |
| | b | With relevant diagrams, explain the internal capacitive effects of BJT. | CO2 | L2 | 5M |

UNIT-III

- | | | | | | |
|---|---|--|-----|----|----|
| 6 | a | Draw the general structure of feedback amplifier and derive the equation for gain of feedback amplifier. | CO3 | L1 | 5M |
| | b | A feedback amplifier has a gain of 1000 without feedback. If 10% of the output voltage is fed back to the input in a negative feedback configuration. Calculate the gain of the amplifier with feedback. | CO3 | L4 | 5M |

OR

- 7 a Construct an RC phase shift oscillator using BJT and derive the expressions for frequency of oscillations and condition for sustained oscillations. CO4 L3 6M
- b Determine the frequency of oscillations when a RC phase shift oscillator has $R=10k\Omega$, $C=0.01\mu F$ and $RC = 2.2 K\Omega$. Also find the minimum current gain needed for this purpose. CO4 L3 4M

UNIT-IV

- 8 a Sketch the collector current waveforms for class A, class B, class AB and class C amplifier stages. CO3 L3 5M
- b The loudspeaker of 8Ω is connected to the secondary of the output transformer of a class A Amplifier. The quiescent collector current is 140 mA. The turns ratio of transformer is 3:1. The collector supply voltage is 10 V. If ac power delivered to the loudspeaker is 0.48 W, assuming ideal transformer, determine (i) AC power developed across primary, (ii) RMS value of load voltage, (iii) RMS value of primary voltage, (iv) RMS value of load current. CO3 L3 5M

OR

- 9 a Compare push-pull Class B and Complementary symmetry Class B power amplifiers. CO3 L3 5M
- b Describe the structure of Power MOSFET. CO3 L2 5M

UNIT-V

- 10 a Compare different types of tuned amplifiers. CO1 L2 5M
- b A single tuned RF amplifier uses a transistor with an output resistance of $50 K\Omega$, output capacitance of 15 pF and internal resistance of next stage is $20 k\Omega$. The tuned circuit consists of 47 pF capacitance in parallel with series combination of $1\mu H$ inductance and 2Ω resistance. Determine resonant frequency, effective quality factor and bandwidth of the circuit. CO3 L3 5M

OR

- 11 a Explain the operation of Schmitt trigger. CO3 L2 5M
- b Determine the value of capacitors to be used in an Astable multivibrator to provide a train pulse $2\mu s$ wide at a repetition rate of 100 KHz, if $R_1 = R_2 = 20k\Omega$. CO5 L3 5M

*** END ***