

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. II Year II Semester Regular Examinations July/August-2025

ANALOG CIRCUITS

(Electrical & Electronics Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions **10 x 2 = 20 Marks**)

- | | | | | | |
|---|---|---|-----|----|----|
| 1 | a | Discuss the need of biasing of a transistor. | CO1 | L2 | 2M |
| | b | Define operating point. | CO1 | L1 | 2M |
| | c | List the characteristics of negative feedback amplifiers. | CO2 | L1 | 2M |
| | d | Sketch the Equivalent circuit of a transistor using h-Parameters. | CO2 | L1 | 2M |
| | e | What is the necessary condition for sustained oscillations? | CO1 | L1 | 2M |
| | f | Define op-amp. | CO1 | L1 | 2M |
| | g | What are the types of Multivibrators? | CO1 | L1 | 2M |
| | h | Define common mode Rejection Ratio. | CO1 | L1 | 2M |
| | i | Draw the pin configuration of 555 timer. | CO2 | L1 | 2M |
| | j | List out the examples of digital phase detectors. | CO1 | L2 | 2M |

PART-B

(Answer all Five Units **5 x 10 = 50 Marks**)

UNIT-I

- | | | | | | |
|-----------|---|--|-----|----|----|
| 2 | a | List out the different types of clipping and clamping circuits. | CO1 | L1 | 5M |
| | b | Explain the concept of DC and AC Load lines and discuss the Criteria for fixing the Q-point. | CO2 | L2 | 5M |
| OR | | | | | |
| 3 | a | Compare the various biasing techniques of a BJT. | CO2 | L2 | 5M |
| | b | Draw the collector to base bias circuit and derive an expression for the stability factor. | CO3 | L3 | 5M |

UNIT-II

- | | | | | | |
|---|--|---|-----|----|-----|
| 4 | | Derive the equations for voltage gain, current gain, Input impedance, and output Impedance for a BJT using Approximate model in CC configuration. | CO3 | L4 | 10M |
|---|--|---|-----|----|-----|

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 5 | a | Sketch the four types of feedback amplifier topologies. | CO2 | L3 | 5M |
| | b | Describe the effect of input resistance for Voltage shunt feedback amplifier. | CO3 | L2 | 5M |

UNIT-III

- | | | | | | |
|---|---|--|-----|----|----|
| 6 | a | Determine the frequency of oscillations when an RC phase shift oscillator has $R=10\text{ k}\Omega$, $C=0.01\mu\text{F}$ and $R_C = 2.2\text{ k}\Omega$. | CO6 | L3 | 5M |
| | b | Explain the working principle of Wein-bridge oscillator using BJT and Derive the expression for frequency of sustained oscillations. | CO3 | L4 | 5M |

OR

- | | | | | | |
|---|---|---|-----|----|----|
| 7 | a | In a Wien bridge oscillator, if the value of R is $100\text{ k}\Omega$ and frequency of oscillation is 10kHz , examine the value of capacitor C. | CO6 | L3 | 6M |
| | b | Draw the schematic symbol of an op-amp and list the different terminals with their features. | CO1 | L1 | 4M |

UNIT-IV

- | | | | | |
|----------|--|------------|-----------|-----------|
| 8 | a Design a differentiator circuit with sine wave input using op-amp. | CO5 | L6 | 6M |
| | b Design an op-amp differentiator that will differentiate an input signal $v_i = 10 \sin 100t$ V. The output voltage v_o must be $10 \cos 100t$ V. Assume $R = 10 \text{ k}\Omega$ and $C = 0.01 \mu\text{F}$. | CO6 | L6 | 4M |

OR

- | | | | | |
|----------|---|------------|-----------|-----------|
| 9 | a Explain the operation of monostable multivibrator using op-amp ,with a neat circuit and its waveforms. | CO6 | L2 | 5M |
| | b Draw the circuit diagram of Non-Inverting comparator & explain its operation. | CO4 | L2 | 5M |

UNIT-V

- | | | | | |
|-----------|--|------------|-----------|-----------|
| 10 | a Explain in detail about R-2R DAC with a neat diagram. | CO4 | L2 | 5M |
| | b Discuss the parameters specifications of DAC/ADC. | CO4 | L2 | 5M |

OR

- | | | | | | |
|----|---|---|-----|----|----|
| 11 | a | Draw a neat circuit of astable multivibrator using 555 IC and explain operation with waveforms. | CO5 | L2 | 5M |
| | b | Explain about PLL principle in detail and block diagram. | CO5 | L2 | 5M |

*** END ***