

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

**B.Tech II Year I Semester Supplementary Examinations November-2020
NETWORK THEORY**

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | |
|---|---|----|
| 1 | a Define Duality & Dual networks. | 2M |
| | b Define Neper and Decibel. | 2M |
| | c Define steady state and transient state. | 2M |
| | d What is the condition for Symmetry in Z and Y parameters? | 2M |
| | e Define Fourier transform. | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | |
|---|---|----|
| 2 | a State and prove Reciprocity theorem. | 5M |
| | b Determine the maximum power delivered to the load in the circuit shown in below | 5M |


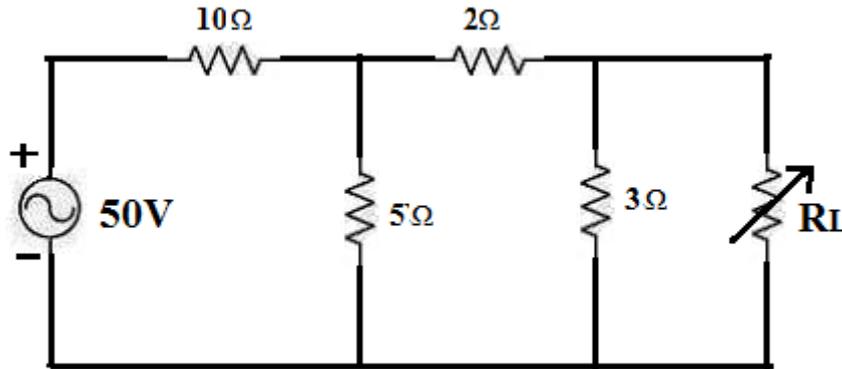


figure.

OR

- | | | |
|---|--|----|
| 3 | a Explain about Mesh analysis and write the steps for writing mesh analysis. | 5M |
| | b Determine the current in 10Ω resistor for the following network by using nodal analysis. | 5M |

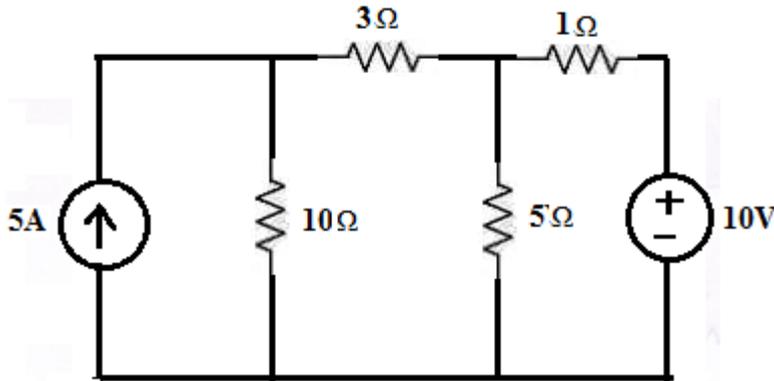

UNIT-II


- | | | |
|---|--|----|
| 4 | a Explain about Quality factor and Bandwidth of Series resonance. | 5M |
| | b Design constant-K band pass filter having a design impedance of 500Ω and cut-off frequencies. $f_1 = 1\text{kHz}$ and $f_2 = 10\text{kHz}$. | 5M |

OR

- 5 a Explain about classification of filters. 5M
- b Explain about Propagation constant and Characteristic impedance in T-network filters. 5M

UNIT-III

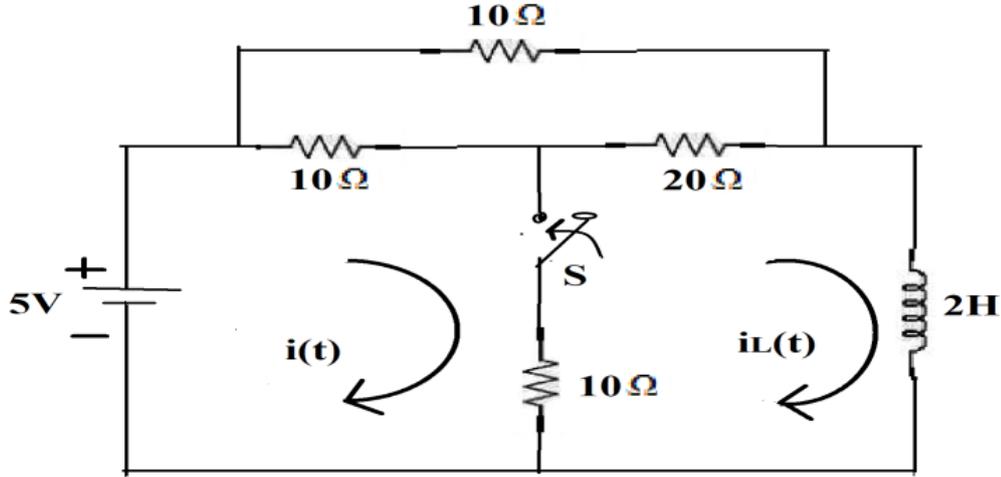- 6 a Derive the Transient Response of series RC-circuit with D.C excitation. 5M
- b The circuit shown in below figure, the switch „S“ is open and the circuit reaches a steady state. At $t=0$, the „S“ is closed. Find the current in the inductor for $t>0$. 5M




OR

- 7 a Derive the Transient Response of Series RC circuits with Pulse excitation. 6M
- b A series RL circuit with $R=30\Omega$ and $L= 15H$ has a constant voltage $V=60v$ applied at $t=0$. Determine the current “I”, voltage across resistor and voltage across inductor. 4M

UNIT-IV

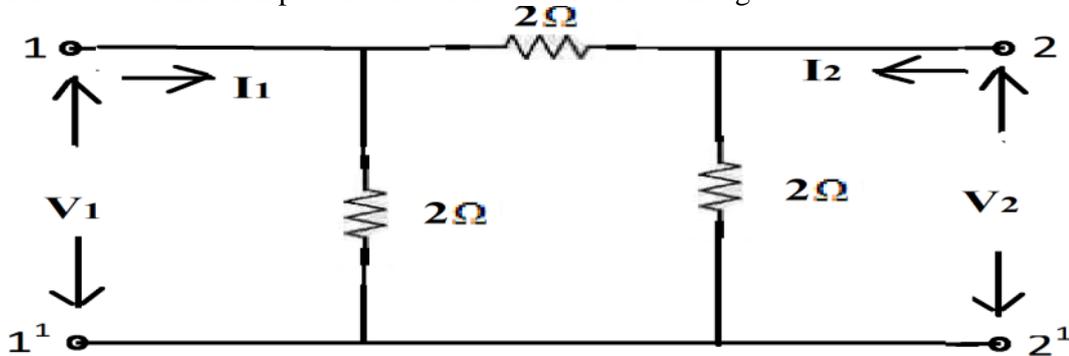- 8 a Explain about Impedance parameters. 6M
- b Find the transmission parameters for the circuit shown in figure. 4M




OR

- 9 a The given ABCD parameters are, $A=2$, $B=0.9$, $C=1.2$, $D= 0.5$. Find Y-parameters. 5M
- b The given Y-parameters are, $Y_{11}= 0.5$, $Y_{12}= Y_{21}= 0.6$, $Y_{22}= 0.9$. Find Impedance parameters. 5M

UNIT-V


10 a Find the Trigonometric Fourier series for the following waveform shown in figure.

5M

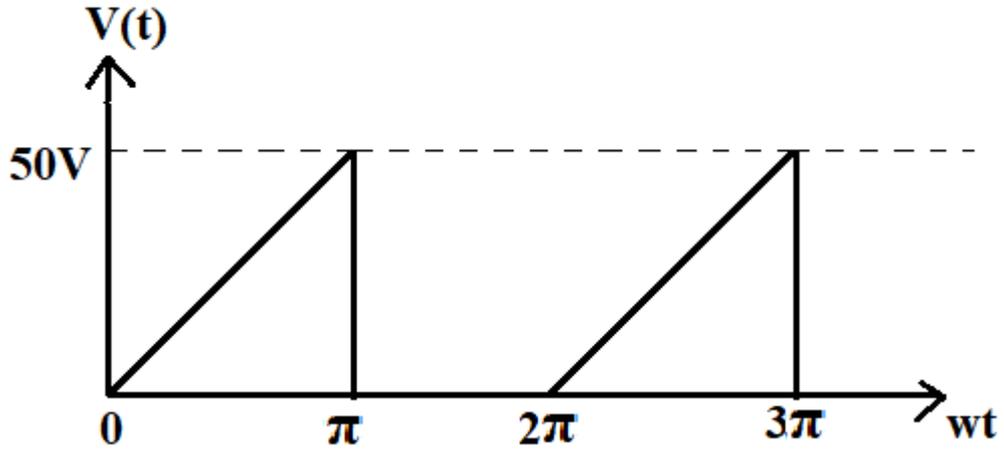

b Find the Exponential Fourier series for the following waveform shown in figure.

5M

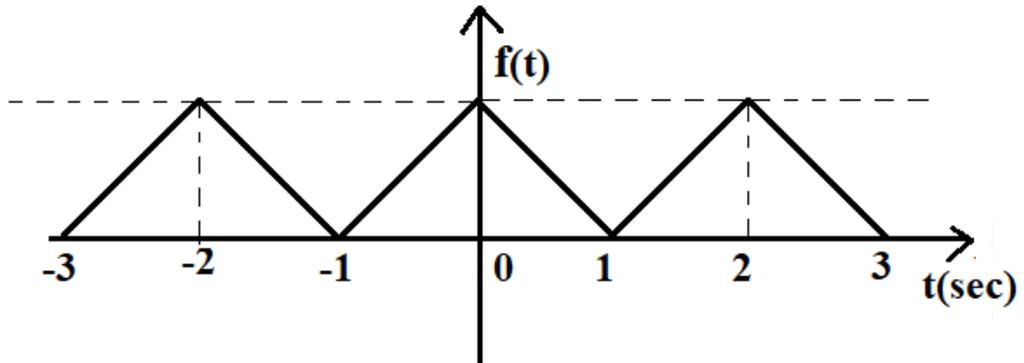


OR

11 a Derive the Exponential form of Fourier series.

5M

b Obtain the Fourier series for the following waveform shown in figure.

5M

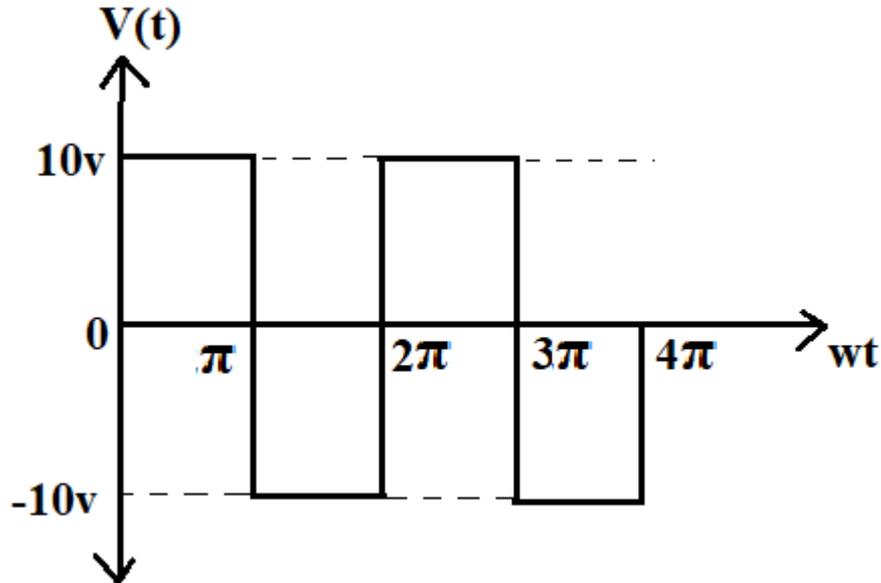

END