



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY
(AUTONOMOUS)**

(Approved by AICTE, New Delhi & Affiliated to JNTUA, Ananthapuramu)
(Accredited by NBA for Civil, EEE, Mech., ECE & CSE)
(Accredited by NAAC with 'A+' Grade)
Puttur -517583, Tirupathi District, A.P. (India)

QUESTION BANK (DESCRIPTIVE)

SUBJECT & CODE:	Analog Electronic circuits(20EC0446)	COURSE & BRANCH:	B.TECH - EEE
YEAR & SEM:	IIYR & I SEM	REGULATION:	R-20

**UNIT –I
FEEDBACK AMPLIFIERS**

1.	a)	Define feedback and illustrate the basic concept of Feedback with suitable block diagram.	[L2][CO1]	[6M]
	b)	List different types of feedback and discuss.	[L1][CO1]	[6M]
2.	a)	Compare positive feedback and negative feedback.	[L2][CO2]	[6M]
	b)	Give the classification of basic amplifiers.	[L2][CO2]	[6M]
3.	a)	Interpret voltage series and current series amplifier topologies with necessary diagrams.	[L2][CO1]	[6M]
	b)	Interpret voltage shunt and current shunt amplifier topologies with necessary diagrams.	[L2][CO1]	[6M]
4.	a)	Summarize the expressions of input and output resistances for a Voltage Series feedback amplifier with necessary derivations.	[L2][CO4]	[8M]
	b)	A voltage series negative feedback amplifier has a voltage gain without feedback of $A=500$, input resistance $R_i=3\text{ k}\Omega$, output resistance $R_o=20\text{ k}\Omega$ and feedback ratio $\beta=0.01$. Calculate the voltage gain A_f , input resistance and output resistance of the amplifier with feedback.	[L3][CO3]	[4M]
5.		Summarize the expressions of Gain, input and output resistances for a Current Series feedback amplifier with necessary derivations.	[L2][CO4]	[12M]
6.		Summarize the expressions of Gain, input and output resistances for a current shunt feedback amplifier with necessary derivations.	[L2][CO4]	[12M]
7.		Summarize the expressions of Gain, input and output resistances for a Voltage Shunt feedback amplifier with necessary derivations.	[L2][CO4]	[12M]
8.	a)	List the characteristics of negative feedback amplifiers.	[L1][CO1]	[6M]
	b)	Explain about Noise reduction and nonlinear distortion in negative feedback.	[L3][CO1]	[6M]
9.	a)	Show that how a negative feedback reduces gain of an amplifier.	[L1][CO1]	[6M]
	b)	An amplifier has open loop gain 1000 and feedback ratio of 0.04, if the open loop gain changes by 10% due to temperature, find the percentage change in the gain of the amplifier feedback.	[L3][CO3]	[6M]
10.	a)	Derive the expression for De-sensitivity (D).	[L1][CO1]	[6M]
	b)	Compare the performance of feedback amplifier.	[L4][CO1]	[6M]

UNIT-II OSCILLATORS

1.	a)	Define Oscillator and explain its principle of operation.	[L2][CO1]	[6M]
	b)	Illustrate the condition for oscillation with suitable diagram.	[L2][CO1]	[6M]
2.	a)	Explain Barkhausen criterion for oscillations with suitable diagram.	[L2][CO1]	[6M]
	b)	Interpret the various types of oscillators.	[L3][CO1]	[6M]
3.	a)	Determine the condition for sustained oscillations for an RC phase shift Oscillator with necessary circuit diagrams.	[L3][CO2]	[8M]
	b)	Determine the frequency of oscillations when an RC phase shift oscillator has $R=100\text{ k}\Omega$, $C=0.01\mu\text{F}$ and $R_C = 2.2\text{ k}\Omega$.	[L3][CO4]	[4M]
4.	a)	Explain the working principle of Wein-bridge oscillator using BJT and Derive the expression for frequency of sustained oscillations.	[L2][CO5]	[8M]
	b)	In a Wien bridge oscillator, if the value of R is $100\text{ k}\Omega$ and frequency of oscillation is 10kHz , examine the value of capacitor C.	[L3][CO3]	[4M]
5.	a)	Draw the circuit diagram of general form of an LC oscillator also give the expression for frequency of oscillation.	[L1][CO1]	[6M]
	b)	Derive the load impedance equation of a generalized LC Oscillator.	[L3][CO1]	[6M]
6.	a)	Draw the circuit diagram of Hartley oscillator using BJT and derive the expression for frequency of oscillations.	[L1][CO1]	[8M]
	b)	In the Hartley oscillator $L_2=0.4\text{mH}$ and $C=0.004\mu\text{F}$. If the frequency of the oscillator is 120kHz , find the value of L_1 . Neglect mutual inductance.	[L3][CO4]	[4M]
7.	a)	Draw the circuit diagram of Colpitts oscillator using BJT and derive the expression for frequency of oscillations.	[L1][CO1]	[8M]
	b)	In the Colpitts oscillator, $C_1=0.2\mu\text{F}$ and $C_2 = 0.02\mu\text{F}$. If the frequency of oscillator is 10kHz , find the value of inductor.	[L3][CO4]	[4M]
8.	a)	Summarize the difference between Hartley and Colpitts oscillator.	[L2][CO4]	[6M]
	b)	In a transistorized Hartley, oscillator the two inductances are 2mH and $20\mu\text{H}$. While the frequency is to be changed from 950 kHz to 2050 kHz . Calculate the range over which the capacitor is to be varied.	[L4][CO4]	[6M]
9.	a)	Explain in detail about the crystal oscillator and mention the expression for its frequency of oscillation.	[L2][CO1]	[8M]
	b)	Compare piezoelectric effect and inverse piezoelectric effect with a neat diagram.	[L2][CO6]	[4M]
10.	a)	Summarize the difference between LC and Crystal oscillator.	[L2][CO4]	[4M]
	b)	Explain the concept of stability in oscillators in detail.	[L2][CO6]	[8M]

UNIT-III OPERATIONAL AMPLIFIER

1.	a)	Explain the basic information and pin configuration of an op-amp.	[L2] [CO1]	[6M]
	b)	Draw the equivalent circuit diagram of Op-amp and list out the ideal characteristics of an operational amplifier.	[L1][CO3]	[6M]
2.	a)	Derive the expression for gain of inverting amplifier.	[L3][CO5]	[6M]
	b)	For an inverting amplifier, $R_1=10\text{k}\Omega$, $R_f=100\text{ k}\Omega$ with input voltage $V_i=1\text{V}$ and a load resistance of $R_L=25\text{ k}\Omega$ is connected to the output terminal. Calculate i) i_1 ii) V_o iii) i_L and iv) load current i_o into the output pin.	[L3][CO4]	[6M]
3.	a)	Derive the expression for gain of non-inverting amplifier.	[L3][CO5]	[6M]
	b)	For an Non-inverting amplifier, $R_1=5\text{k}\Omega$, $R_f=20\text{ k}\Omega$ with input voltage $V_i=1\text{V}$ and a load resistance of $R_L=5\text{ k}\Omega$ is connected to the output terminal. Calculate i) V_o ii) A_{CL} iii) i_L and iv) load current i_o indicating proper direction of flow.	[L3][CO4]	[6M]
4.	a)	What is voltage follower? What are its features and applications?	[L1][CO1]	[6M]
	b)	Estimate the gain of a Differential amplifier.	[L4][CO2]	[6M]
5	a)	What are the four different configuration of differential amplifier?	[L1][CO1]	[6M]
	b)	Derive the expression for gain of Differential amplifier with two op-amps.	[L3][CO5]	[6M]
6.	a)	Define the terms differential mode gain, common mode gain, CMRR.	[L1][CO2]	[6M]
	b)	Explain DC characteristics of op-amp.	[L2][CO3]	[6M]
7.	a)	Illustrate the following terms with neat diagram i) Input bias current ii) Input offset current.	[L3][CO1]	[6M]
	b)	Illustrate the following terms with neat diagram i) Input offset voltage ii) Thermal drift.	[L3][CO1]	[6M]
8.	a)	Explain AC characteristics of op-amp.	[L2][CO5]	[8M]
	b)	Draw and explain frequency response of practical op-amp.	[L2][CO1]	[6M]
9.	a)	What is frequency compensation and explain how the frequency response is varied with respect to External Compensation technique.	[L1][CO6]	[8M]
	b)	Explain how the frequency response is varied with respect to internal Compensation technique.	[L2][CO5]	[4M]
10.	a)	Explain the term slew rate and illustrate the importance in op-amp circuits.	[L2][CO3]	[6M]
	b)	An op-amp has a slew rate of $2\text{V}/\mu\text{s}$. What is the maximum frequency of an output sinusoidal its peak value of 5V at which the distortion sets in due to the slew rate limitation?	[L1][CO4]	[4M]

UNIT-IV APPLICATIONS OF THE OP-AMP

1.	a)	Design and explain the operation of inverting summing amplifier.	[L3][CO3]	[6M]
	b)	Design an inverting adder circuit using an op-amp to get the output expression as $V_o = -(0.1V_1 + V_2 + 10V_3)$, Where V_1, V_2 and V_3 are the inputs.	[L3][CO3]	[6M]
2.	a)	Design and explain the operation of non-inverting summing amplifier.	[L3][CO3]	[6M]
	b)	The op-amp non-inverting summing circuit has the following parameters $V_{CC} = +15\text{ V}$, $V_{EE} = -15\text{ V}$, $R = R_1 = 1\text{ k}\Omega$, $R_f = 2\text{ k}\Omega$, $V_1 = +2\text{ V}$, $V_2 = -3\text{ V}$, $V_3 = +4\text{ V}$. Determine the output voltage V_o .	[L3][CO3]	[6M]
3.	a)	Draw the circuit of a subtractor using op-amp and derive the expression for voltage gain.	[L3][CO1]	[6M]
	b)	Draw an op-amp circuit whose output is $V_o = (V_3 + V_4) - (V_1 + V_2)$.	[L3][CO1]	[6M]
4.	a)	Explain the operation of differentiator using op-amp with a neat circuit diagram.	[L2][CO5]	[6M]
	b)	Draw the input-output waveforms and frequency response of differentiator.	[L1][CO1]	[6M]
5.	a)	Design a differentiator to differentiate an input signal that has $f_{\max} = 100\text{ Hz}$.	[L2][CO5]	[6M]
	b)	Explain the operation of integrator using op-amp with a neat circuit diagram.	[L3][CO5]	[6M]
6.	a)	Draw the input-output waveforms and frequency response of integrator.	[L1][CO1]	[6M]
	b)	Explain sample and hold circuit using op-amp.	[L2][CO1]	[6M]
7.	a)	Draw a neat circuit of astable multivibrator using op-amp and explain operation with waveforms.	[L2][CO2]	[6M]
	b)	Define the duty cycle. Identify the percentage of duty cycle if $T_{\text{on}} = 0.6\text{ msec}$, $T_{\text{off}} = 0.4\text{ msec}$	[L3][CO4]	[6M]
8.	a)	Derive the equation for frequency of oscillation of astable multivibrator using op-amp.	[L3][CO4]	[6M]
	b)	Calculate the frequency of oscillation for an astable multivibrator having $R_2 = 10\text{ k}\Omega$, $R_1 = 8.6\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$ and $C = 0.01\text{ }\mu\text{F}$.	[L4][CO4]	[6M]
9.	a)	Explain the operation of monostable multivibrator using op-amp, with a neat circuit and its waveforms	[L2][CO2]	[6M]
	b)	Derive the equation for pulse width of the monostable multivibrator using op-amp.	[L3][CO4]	[6M]
10.		Explain the operation of triangular wave generator using op-amp, with a neat circuit diagram and its waveforms.	[L2][CO3]	[12M]

UNIT-V
ACTIVE FILTERS AND CONVERTERS USING OP-AMP

1.	a)	Define active filter and give its characteristics.	[L4][CO2]	[6M]
	b)	Explain the first order low pass butter worth filter with a neat circuit diagram.	[L2][CO2]	[6M]
2.	a)	Draw the frequency response of filters.	[L3][CO1]	[6M]
	b)	Explain the first order high pass butter worth filter with a neat circuit diagram.	[L2][CO2]	[6M]
3.		Design a low pass filter at a cut-of frequency of 15.9kHz with pass band gain of 1.5 and draw the frequency response.	[L3][CO3]	[12M]
4.		Design a high pass filter at a cut-of frequency of 10kHz with pass band gain 1.5 and draw the frequency response.	[L3][CO3]	[12M]
5.	a)	Explain the weighted resistor DAC with a neat diagram.	[L2][CO2]	[6M]
	b)	An 8-bit Analog to Digital converter has a supply voltage of +12 volts. Calculate: (i) The voltage step size for LSB. (ii) The value of analog input voltage for a digital output of 01001011.	[L4][CO4]	[6M]
6.	a)	Explain in detail about R-2R DAC with a neat diagram.	[L2][CO3]	[6M]
	b)	The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “10110111”?	[L1][CO4]	[6M]
7.	a)	Draw the circuit diagram of inverted R-2R DAC and explain its operation.	[L2][CO2]	[6M]
	b)	Design an inverted R-2R ladder DAC for digital input word 001.	[L3][CO4]	[6M]
8.	a)	Explain about the flash type ADC using op-amp.	[L2][CO1]	[6M]
	b)	Summarize the truth table for a flash type op-amp ADC using 8 by 3 priority encoder.	[L2][CO4]	[6M]
9.		Draw the circuit diagram of Dual Slope ADC and explain its working with neat sketches.	[L2][CO2]	[12M]
10.		Discuss the parameter and specifications of DAC/ADC.	[L2][CO1]	[12M]

Prepared by

Mrs. D. Sakunthala, Assistant Professor,

Mrs. P Saranya, Assistant Professor,

Department of ECE,

SIETK, Puttur.