SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: Electronic Devices and Circuits(23EC0402) Course & Branch: B.Tech.–ECE Regulation: R23

Year & Sem: II-B.Tech.& I-Sem.

1.	a)	Define efficiency of a rectifier.	[L1][CO4]	[2M]
	b)	Define regulation and write formula to find regulation of a rectifier.	[L1][CO4]	[2M]
	c)	Define clipper and list types.	[L1][CO2]	[2M]
	d)	List the applications of clampers.	[L1][CO2]	[2M]
	e)	Formulate the Diode current equation.	[L1][CO2]	[2M]
2.	a)	Describe the construction of PN Junction Diode.	[L2][CO1]	[4M]
	b)	Illustrate the working of a PN Junction diode under forward bias and reverse bias with neat diagrams and draw VI characteristics	[L2][CO1]	[6M]
3.	a)	Discuss the effect of temperature on V-I characteristics of a PN Junction Diode.	[L2][CO2]	[5M]
	b)	When a reverse bias is applied to a germanium PN Junction Diode, the reverse saturation current at room temperature is 0.3μ A. Determine the current flowing in the diode when $0.3V$ forward bias is applied at room temperature.	[L3][CO3]	[5M]
4.	a)	Discuss about the forward and reverse resistances of a PN junction diode.	[L2][CO1]	[5M]
	b)	Calculate the forward resistance of a PN Junction Diode when the forward current is 5mA at $T = 300$ K. Assume Silicon diode.	[L3][CO3]	[5M]
5.	a)	 Discuss the following terms i) Transition capacitance ii) Diffusion capacitance of a PN Junction Diode. 	[L3][CO2]	[5M]
	b)	Draw the circuit diagram of a Half Wave Rectifier and explain its operation with the help of waveforms.	[L2][CO4]	[5M]
6.	a)	Derive the expressions for Average DC Voltage, RMS Value of voltage, DC Output Power and AC input Power, Efficiency and Ripple factor for a Half Wave Rectifier.	[L2][CO4]	[5M]
	b)	A Half Wave Rectifier is supplied from a 230V, 50 Hz supply with a step-down ratio of 3:1 to a resistive load of $10k\Omega$. The diode forward resistance is 75Ω while transformer secondary is 10Ω . Calculate maximum, average, RMS values of current, DC output voltage, efficiency of rectification.	[L4][CO4]	[5M]
7.	a)	Compare Half Wave, Full Wave and Bridge Wave rectifiers.	[L4][CO4	[5M]
	b)	A Full Wave Rectifier circuit is fed from a transformer having a	[L4][CO4]	[5M]
		center-tapped secondary winding. The RMS voltage from either end of secondary to center tap is 30V. If the diode forward		

UNIT –I PN JUNCTION DIODE AND SPECIAL DIODES

		resistance is 2Ω and that of the half secondary is 8Ω , for a load		
		of 1 K Ω . Calculate DC power delivered to the load, efficiency of		
		rectification.		
8.	a)	Design the Positive and Negative Diode Clippers and explain	[L2][CO5]	[5M]
		with neat waveforms.		
	b)	What is a Clamper circuit? Describe about positive and negative	[L2][CO4]	[5M]
		clampers with neat circuit diagram.		
9.	a)	Discuss the characteristics of Photo diode with its symbol.	[L3][CO2]	[3M]
	b)	With neat diagram explain working of SCR and draw the VI	[L1][CO2]	[7M]
		characteristics.		
10.	a)	Compare the characteristics of LCD with LED.	[L4][CO1]	[3M]
	b)	With basic structure, symbol and equivalent circuit explain	[L2][CO2]	[7M]
		working of UJT and draw characteristics.		
11	a)	Define the basic principle of Varactor diode and list its	[L1][CO1]	[3M]
		applications		
	b)	Draw the circuit symbol of Tunnel diode. Explain the Volt-	[L2][CO2]	[7M]
		Ampere (V-I) characteristics		

-				
1	SIPOI	LAR JUNCTION TRANSISTOR CHARACTERISTICS AND E	BIASING	
1.	a)	Define BJ1 and Draw its symbol.		
	D)	List the types of BJT and operating regions.		
	c)	List applications of BJ1.		
	d)	Discuss the need of blasing.		
	e)	List out BJT specifications.		
2.	a)	Discuss the operation of NPN and PNP transistor with diagram.		
	D)	with a neat diagram, explain now a transistor acts as an	[L4][CO3]	[5]/1]
2		amplifier and switch. Derive the relation emong g , θ and Σ of a Transiston		[6]/[]
3.	a)	Let the here connect in a transition is 200 A relies the arritten		
	D)	If the base current in a transistor is 20μ A when the emitter		[4]\1]
		the collector current		
1	9) 	With next circuit diagram explain the Input and Output	[I 3][CO4]	[5M]
7.	<i>a)</i>	characteristics of a BIT in CB Configuration		
	b)	Differentiate among CE_CB & CC configurations	[L2][C04]	[5M]
5	a)	With neat circuit diagram explain the Input and Output	[L2][C04]	[5M]
	<i>u)</i>	characteristics of a BJT in CC Configuration.		
	b)	For a transistor, the leakage current is 0.1µA in CB	[L3][CO3]	[5M]
	.~,	configuration, while it is 19 μ A in CE configuration. Calculate α	[][]	[]
		& β of the same transistor.		
6.	a)	Discuss the Input and Output characteristics of a BJT in CE	[L3][CO4]	[6M]
		Configuration. Indicate the regions of operations in the output		
		characteristics.		
	b)	Explain the limits of operation in BJT.	[L3][CO1]	[4M]
7.	a)	Explain the concept of DC and AC Load lines and discuss the	[L2][CO2]	[5M]
		criteria for fixing the Q-point.		
	b)	Mention different types of Biasing a Transistor and explain the	[L2][CO5]	[5M]
		Fixed Bias of a Transistor.		
8.	a)	Explain Collector to Base bias of a Transistor with neat circuit	[L2][CO4]	[6M]
	•	diagram.		543 (2)
	b)	Compare and contrast the characteristics of NPN and PNP	[L3][CO2]	[4M]
		transistors		F 4 N 471
9.	a) b)	Explain self-bias of a Transistor with heat circuit diagram.	[L2][C02]	[4]VI]
10	0) 0)	Compare the various biasing techniques of a DIT	$[L_2][CO4]$	
10.	a) b)	Compare the values biasing techniques of a D_{11} .		
	0)	Consider the sen-bias circuit where $vcc = 22.5$ volts, KC =5.6kO R ₂ = 10kO and P ₄ = 00kO bf ₂ = 55 V ₂ = -0.6V the		[01 /1]
		-5.0 Ks2, K ₂ = 10 Ks2 and K ₁ = 70 Ks2, file = 55, V _{BE} = 0.0 V. life transistor operates in active region. Determine i) Operating point		
		i) stability factor		
11	a)	Discuss Thermal Runaway and Thermal Resistance	[L1][CO2]	[6M]
11.	b)	Discuss the condition for achieving Thermal Stability	[L2][CO2]	[4M]
1	~,		L1L ~ ~ = 1	L ****

1	a)	What is the trans conductance g_m in a BJT?	[L1] [CO1]	2M
	b)	How is r_{π} (input resistance) calculated in the hybrid- π model?	[L2] [CO1]	2M
	c)	List out the characteristics of CE amplifier.	[L1] [C01]	2M
	d)	Express the open circuit over all voltage gain of BJT amplifier.	[L2] [C01]	2M
	e)	Name the applications of CC amplifier.	[L1][C01]	2M
2	a)	Discuss the purpose of small-signal analysis in BJT circuits.	[L2] [C01]	[5M]
_	b)	Explain the thermal voltage V_T and how does it affect the small-signal model?	[L2] [C01]	[5M]
3	a)	Derive the transconductance g_m for a given collector current I _C	[L3] [CO2]	[5M]
-	b)	Determine base current and input resistance at Base of BJT.	[L3] [C01]	[5M]
4	a)	Determine Emitter current and input resistance at Emitter of BJT.	[L3] [CO2]	[5M]
_	b)	Describe the process of finding the DC operating point (quiescent point) of a	[L2] [C01]	[5M]
		BJT.		L' J
5		Evaluate a voltage gain for transistor amplifier as shown in figure, assume β =100	[L5] [CO2]	[10M]
		LION		
		Vcc oftov		
		20 010		
		ZKC = 3K-1-		
		Paga IDAKA I		
		KBB = 100 m		
		ANM		
		NIS CO		
		$V_i^{\epsilon}(T)$		
		Ý.		
		Describe the law components of the hybrid rimedal for a DIT	[[1] [CO2]	[5] (7)
0	a) b)	List out the applications of Small signal Equivalent signation		[51VI]
7	D)	List out the applications of sinall-signal Equivalent circuits.		[51VI]
'	a)	Compare the T model and the ball of a model.		
	b)	Compare the 1-model and the hybrid- π model.	[L4] [CO3]	[5M]
8	a)	Discuss about separating the signal and the DC quantities with suitable	[L2] [CO4]	[6M]
	•	diagrams.		E 43 63
•	b)	Define voltage gain and derive A_v for CE amplifier.		[4M]
9	a)	Evaluate the small-signal voltage gain $A_{v_i} \kappa_i$ and κ_0 of a common-emitter amplifier	[L4] [CO4]	
		Without an emitter resistor $\mathbf{R}_{\mathbf{F}}$ with equivalent circuit		
	b)	List out the characteristics of CE amplifier with emitter resistance.	[L1] [CO1]	[3M]
10	a)	Derive the small-signal voltage gain $A_v R_i$ and R_o of a common-Base	[L2] [CO4]	[7M]
		amplifier with	[][001]	[]
		Equivalent circuit.		
	b)	Design the small-signal, common-collector amplifier with equivalent circuit	[L2] [CO2]	[3M]
11		For the common emitter amplifier shown in figure Vcc = 9V.R ₁ = 27 k Ω . R ₂ =	[L3] [CO4]	[10M]
		15 k Ω , R _E =1.2 k Ω and R _c = 2.2 k Ω . The transistor has β =100 , V _A =100 V.		L]



R23

UNIT-IV

Junction Field Effect Transistor and MOS Field Effect Transistors

	1			
	a)	State the application of JFET	[L1][CO2]	[2M]
	b)	Define Pinchoff Voltage.	[L1][CO2]	[2M]
	c)	Classify the types of JFET with its symbols.	[L1][CO2]	[2M]
1.	d)	What is the principle of a MOSFET?	[L1][CO2]	[2M]
	e)	Draw the CMOS structure.	[L1][CO2]	[2M]
2	a)	What is meant by FET? List important features of FET.	[L1][CO2]	[4M]
۷.	b)	Explain the construction and working of N-channel JFET.	[L2][CO2]	[6M]
2		Discuss the Transfer and output characteristics of N-channel	[L2] [CO4]	[10M]
э.		JFET with neat sketches.		
4.	a)	How do you fix the Q point for FET?	[L2] [CO2]	[4M]
	b)	Distinguish between BJT and FET.	[L5] [CO2]	[6M]
	a)	Discuss how a JFET works as a voltage variable resistor.	[L4] [CO3]	[6M]
5.	b)	Classify the types of MOSFET and draw their symbols.	[L2][CO3]	[4M]
	,	5 51 5		
	a)	Explain the construction & operation of an enhancement type	[L2] [CO2]	[6M]
6	<i>.</i>	NMOS Transistor.		
0.	b)	Plot the V-I Characteristics of an n-channel enhancement	[L2] [CO2]	[4M]
		MOSFET.		
	a)	Design the circuit in Fig. below to obtain a current I_D of 80	[L2] [CO2]	[6M]
		μ A. Find the value required for R, and find the dc voltage V _D .		
		Let the NMOS transistor have $V_t = 0.6 \text{ V}$, $\mu_n C_{ox} = 200$		
		μ A/V ² .L = 0.8 μ m, and W = 4 μ m. Neglect the channel-length		
_		modulation effect (i.e., assume $\lambda = 0$).		
7.		$V_{D/2} = +3V$		
		$I_D \neq \mathbf{S}_R$		
		- 1		
	b)	-	[I 4] [CO5]	[5M]
	U)	Design a switch using a MOSFET.	$\frac{[L4][C03]}{[L4][C05]}$	[5]VI]
8.	a) b)	Consider a manufacture for a big to the set of the set	$\frac{[L4][C03]}{[L3][C03]}$	
	D)	Consider a process technology for which $L_{min} = 0.4 \ \mu m$, $t_{ox} = 8 \ nm \ w = 450 \ m^2/M \ a \ ond \ M = 0.7 \ M$	[L3][C03]	
		(i) Calculate C_{ov} and k_{-} .		
		(i) For a MOSEET with $W/I = 8 \text{ µm}/0.8 \text{ µm}$ calculate the		
		(i) FOL a WOSFET with $W/L = 0 \mu H/0.0 \mu H$, calculate the values of V as and V by \cdot needed to operate the transistor in		
		values of VGS and VDSmin needed to operate the transistor in the saturation region with a decurrent $I_{\rm D} = 100 \text{ u}$ A		
		(iii) For the device in (ii) calculate the value of V_{cc} required		
		to cause the device to operate as a $1000-\Omega$ resistor for very		
		small V_{DC}		
	<u>a)</u>	Explain the biasing technique by fixing V_{cs} without source	[L1] [CO2]	[5M]
9	ч)	resistance for MOSFET amplifier.		[~1,1]
<i>.</i>	b)	Explain the biasing technique using drain to gate feedback	[L2] [CO4]	[5M]
	,	resistor for MOSFET amplifier.		[~11#]
	a)	Explain the concept of modeling of Body Effect.	[L2] [CO2]	[4M]
10.	b)	Distinguish between Depletion MOSFET and Enhancement	[L5] [CO2]	[6M]
		MOSFET.		·1
44		Discuss the characteristic parameters of the JFET and show	[L2] [CO3]	[10M]
11		the relation among the JFET parameters u. rd and gm.		

UNIT- V

MOSFET SMALL SIGNAL OPERATION MODELS

1	a)	List the small-Signal Parameters of MOSFET.	[L1][CO1]	[2M]
	b)	What is Small-Signal Analysis of MOSFET?	[L1][CO4]	[2M]
	c)	Define Transconductance.	[L1][CO5]	[2M]
	d)	Draw an alternative representation of the T model.	[L1][CO5]	[2M]
	e)	List the applications of the Small-Signal Equivalent Circuits.	[L1][CO2]	[2M]
2	a)	Demonstrate the Small-Signal Operation of the MOSFET amplifier.	[L2][CO5]	[6M]
	b)	Explain the separating the DC Analysis and the Signal Analysis.	[L2][CO4]	[4M]
3			[L3][CO3]	[10M]
		V_{DD}		
		▲		
		$i_{D} \vee \langle R_{D} \rangle$		
		V_{GS} –		
		For the above amplifier let $V_{DD} = 5V$, $P_D = 10KO$, $V_c = 1V$, $K^2 = 20$, U_c		
		For the above amplifier, let $V_{DD} = 5V$, $K_D = 10KS2$, $V_t = 1V$, $K_n = 20 \mu$ Δ/V^2		
		$W/L = 20$, VGS=2V, and $\lambda = 0$. Determine		
		i) the dc current I_D and dc voltage V_{DS}		
		ii) g _m		
		iii) Voltage gain		
4		1v) If $V_{GS} = 0.2 \sin wt$, find V_{DS}		[10]/[]
4		i) Neglecting the dependence of in on yog in saturation	[L2][C03]	
		i) Including the effect of channel length modulation		
		modulated by output resistance $r_0 = VA /I_D$		
5	a)	Define the MOSFET Transconductance g_m with mathematical expression.	[L1][CO5]	[6M]
	b)	A MOSFET is to operate at $I_D = 0.1$ mA and is to have $g_m = 1$ mA/ V. If	[L3][CO3]	[4M]
		$\mathbf{K}_{n}^{\prime} =$	_	
		$50 \mu \text{ A/V}^2$, Compute the required W/L ratio and the over drive voltage.		[10]
6		Develop and Illustrate the T Equivalent-Circuit Model for the MOSFET.	[L3][C05]	
/	a)	Evaluate the overall voltage gain of the Common-Source Amplifier with a	[L5][C05]	
		Source Resistance with suitable circuits.		
	b)	Build the equivalent circuit with the MOSFET represented by its T-	[L3][CO5]	[4M]
	Ĺ	Model.		
8	a)	Construct and Evaluate the overall voltage gain of the Common-Gate	[L5][CO5]	[6M]
		(CG) Amplifier with bigging circuit amitted		
	b)	Amplifier with diasing circuit of the CG amplifier with the MOSEET	II GICOSI	[4 M]
		replaced		L≞ [⊥] ≬T]
L	1		1	1

COURSE CODE: 23EC0402

R23

		with its T-Model.		
9	a)	Illustrate the need for Voltage Buffers or unity gain buffer amplifier with	[L3][CO5]	[6M]
		figures.		
	b)	List the important features of Source Follower.	[L1][CO5]	[4M]
10	a)	A CS amplifier utilizes a MOSFET biased at $I_D = 0.25Ma$ with $V_{OV} =$	[L4][CO3]	[6M]
		0.25V and $R_D = 20k\Omega$. The device has $V_A = 50V$. The amplifier is fed		
		with a source having $R_{sig} = 100K\Omega$, and a $20k\Omega$ load is connected to		
		the output. Calculate		
		R_{in} , A_{vo} , R_o , A_v and G_v .		
	b)	Compare the various parameters of CS, CG & CD amplifiers.	[L4][CO6]	[4M]
11	a)	Inspect the characteristic Parameters of the Source Follower with figures.	[L4][CO4]	[6M]
	b)	Illustrate the MOSFET Transconductance gm with graphical construction.	[L3][CO5]	[4M]

Prepared by D Muneendra, Madhu D & K Manjunath Department of ECE, SIETK, Puttur.