



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road– 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: ADVANCED POWER ELECTRONICS

Course & Branch: M.TECH. IN POWER ELECTRONICS

Year & Sem: I-M.Tech & II Sem



Regulation: R25




UNIT –I

HIGH-POWER SEMICONDUCTOR DEVICES

1	a	Explain the different types of power diodes briefly.	[L2][CO1]	[4M]
	b	Explain the diode reverse recovery characteristics in detail.	[L2][CO1]	[6M]
2	a	Explain the construction and working of Power MOSFET.	[L2][CO1]	[5M]
	b	Explain the characteristics of Power MOSFET.	[L2][CO1]	[5M]
3	a	Explain the construction and working of Insulated Gate Bipolar Transistor (IGBT).	[L3][CO1]	[5M]
	b	Explain the characteristics of Insulated Gate Bipolar Transistor (IGBT).	[L3][CO1]	[5M]
4		Explain the Switching Characteristics during Turn-on and Turn-off of Silicon-Controlled Rectifier (SCR)	[L3][CO1]	[10M]
5	a	Explain the characteristics of Gate Turn Off (GTO) Thyristor.	[L3][CO1]	[6M]
	b	Compare Gate Turn Off (GTO) Thyristor and Silicon-Controlled Rectifier (SCR).	[L4][CO1]	[4M]
6	a	Explain the characteristics of Gate Commutated Thyristor (GCT).	[L4][CO1]	[5M]
	b	Compare Silicon-Controlled Rectifier (SCR), Gate Turn Off (GTO) Thyristor and Gate Commutated Thyristor (GCT).	[L3][CO2]	[5M]
7		Explain the two-transistor model of Silicon-Controlled Rectifier.	[L3][CO2]	[10M]
8		Explain the operation of series connected Silicon-Controlled Rectifier.	[L2][CO2]	[10M]
9		What are the main Causes of Voltage Unbalance. Explain the voltage Equalization for GCTs.	[L2][CO2]	[10M]
10	a	A string of four series-connected thyristors is provided with static and dynamic equalizing circuits. This string has to withstand an off-state voltage of 10 kV. The static equalizing resistance is $25000\ \Omega$ and the dynamic equalizing circuit has $R_c = 40\ \Omega$ and $C = 0.08\ \mu F$. The leakage currents for four thyristors are 21 mA, 25 mA, 18 mA and 16 mA respectively. Determine voltage across each SCR in the off-state and the discharge current of each capacitor at the time of turn-on.	[L2][CO2]	[5M]
	b	Explain the voltage Equalization for IGBTs.	[L2][CO2]	[5M]

UNIT –II
RESONANT PULSE INVERTERS

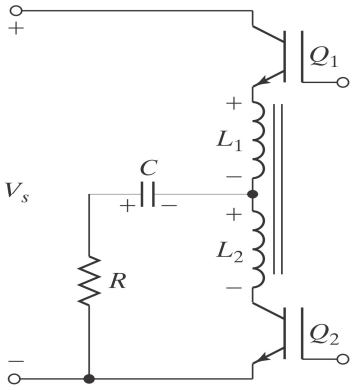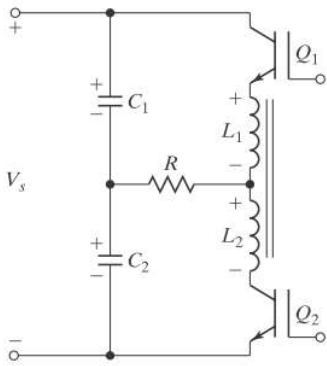1	Explain in detail various modes of operation of Series resonant Inverters with unidirectional Switches.	[L3][CO3]	[10M]
2	The series resonant inverter in Figure 7.2 has $L_1 = L_2 = L = 50 \mu\text{H}$, $C = 6 \mu\text{F}$, and $R = 2 \Omega$. The dc input voltage is $V_s = 220 \text{ V}$ and the frequency of output voltage is $f_o = 7 \text{ kHz}$. The turn-off time of transistors is $t_{\text{off}} = 10 \mu\text{s}$. Determine (a) the available (or circuit) turn-off time t_{off}, (b) the maximum permissible frequency f_{max}, (c) the peak-to-peak capacitor voltage V_{pp}, and (d) the peak load current. (e) Sketch the instantaneous load current $i_o(t)$, capacitor voltage $v_c(t)$, and dc supply current $i_s(t)$. Calculate (f) the rms load current I_o; (g) the output power P_o; (h) the average supply current I_s; and (i) the average, peak, and rms transistor currents. 	[L3][CO3]	[10M]
3	The half-bridge resonant inverter in Figure below, is operated at an output frequency, $f_o = 7 \text{ kHz}$. If $C_1 = C_2 = C = 3 \mu\text{F}$, $L_1 = L_2 = L = 50 \mu\text{H}$, $R = 2 \Omega$, and $V_s = 220 \text{ V}$, determine (a) the peak supply current I_{ps}, (b) the average transistor current I_A, and (c) the rms transistor current I_R. 	[L4][CO3]	[10M]
4	Explain with necessary waveforms, the operation of a series resonant Inverters with Bidirectional Switches	[L3][CO3]	[10M]
5	The resonant inverter in Figure below has $C = 2 \mu\text{F}$, $L = 20 \mu\text{H}$, $R = \infty$, and $V_s = 220 \text{ V}$. The switching time of the transistor is $t_{\text{sw}} = 12 \mu\text{s}$. The output frequency is $f_o = 20 \text{ kHz}$. Determine (a) the peak supply current I_p, (b) the average device current I_A, (c) the rms device current I_R, (d) the peak-to-peak capacitor voltage V_{pp}, (e) the maximum permissible output frequency f_{max}, and (f) the average supply current I_s.	[L2][CO3]	[10M]

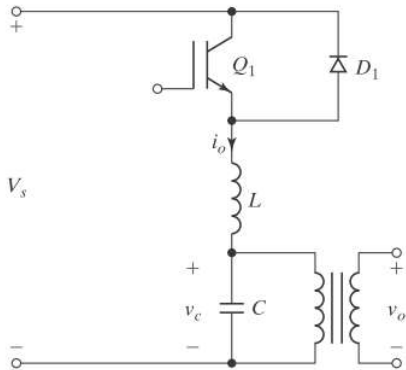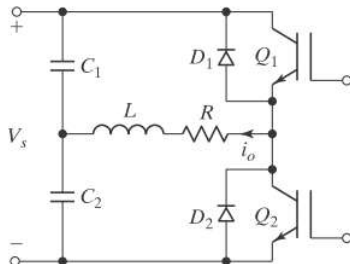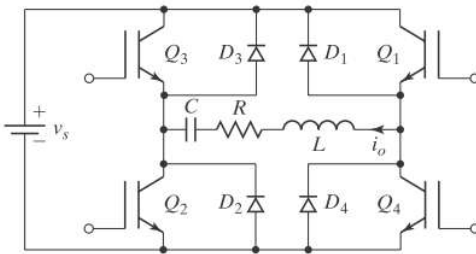			
6	The half-bridge resonant inverter in Figure 7.8a is operated at a frequency of $f_o = 3.5$ kHz. If $C_1 = C_2 = C = 3 \mu\text{F}$, $L_1 = L_2 = L = 50 \mu\text{H}$, $R = 2 \Omega$, and $V_s = 220$ V, determine (a) the peak supply current I_p, (b) the average device current I_A, (c) the rms device current I_R, (d) the rms load current I_o, and (e) the average supply current I_s.  (a) Circuit	[L2][CO3]	[10M]
7	The full-bridge resonant inverter in Figure below is operated at a frequency, $f_o = 3.5$ kHz. If $C = 6 \mu\text{F}$, $L = 50 \mu\text{H}$, $R = 2 \Omega$, and $V_s = 220$ V, determine (a) the peak supply current I_p, (b) the average device current I_A, (c) the rms device current I_R, (d) the rms load current I_o, and (e) the average supply current I_s.  (a) Circuit	[L2][CO3]	[10M]
8	Explain the frequency response of series resonant inverter for series loaded inverter.	[L4][CO3]	[10M]
9	Explain the operation of parallel resonant inverter.	[L2][CO3]	[10M]
10	Explain the various modes of operation of Class-E resonant inverter	[L3][CO3]	[10M]

UNIT -III
RESONANT CONVERTERS

1	a	Explain various switch configurations for Zero current switching resonant converters.	[L2][CO4]	[5M]
	b	The ZCS resonant converter of Figure below delivers a maximum power of $P_L = 400$ mW at $V_o = 4$ V. The supply voltage is $V_s = 12$ V. The maximum operating frequency is $f_{\max} = 50$ kHz. Determine the values of	[L2][CO4]	[5M]

		Land C . Assume that the intervals t_1 and t_3 are very small, and $x = 1.5$.		
2		Explain the various modes of operation of L-type Zero current switching resonant Converter	[L3][CO4]	[10M]
3		Explain the various modes of operation of M-type Zero current switching resonant Converter	[L3][CO4]	[10M]
4		Explain the various modes of operation of Zero voltage switching resonant Converter	[L3][CO4]	[10M]
5	a	Explain the comparison between Zero current switching and Zero voltage switching resonant converters.	[L4][CO4]	[5M]
	b	What is the principle of zero-current-switching (ZCS) resonant converters?	[L4][CO4]	[5M]
6		Explain the various modes of operation of Two quadrant ZVS resonant converters	[L2][CO4]	[10M]
7		Explain single phase Resonant dc link inverters with necessary waveforms.	[L3][CO4]	[10M]
8		Explain three phase Resonant dc link inverters with necessary waveforms.	[L2][CO4]	[10M]
9		What are the advantages and limitations of Zero current switching converters?	[L2][CO6]	[10M]
10		What are the advantages and limitations of Zero voltage switching converters?	[L2][CO6]	[10M]

UNIT -IV MODULATION TECHNIQUES

1	Explain sinusoidal pulse width modulation scheme with necessary wave forms	[L2][CO5]	[10M]
2	Discuss the concepts of harmonic content in two level inverter waveform and over modulation.	[L3][CO5]	[10M]
3	Explain the concept of space vectors and switching states of space vector modulation.	[L3][CO5]	[10M]
4	Explain Dwell time calculation in space vector modulation.	[L2][CO5]	[10M]
5	Explain the concept of modulation index in space vector modulation.	[L3][CO5]	[10M]
6	Explain the concept of switching sequence in space vector modulation.	[L3][CO5]	[10M]
7	Explain how to eliminate even order harmonics using modified space vector modulation.	[L2][CO6]	[10M]
8	Explain Bipolar Pulse-Width Modulation in Single-phase H-bridge inverter.	[L2][CO6]	[10M]
9	Explain Unipolar Pulse-Width Modulation in Single-phase H-bridge inverter.	[L2][CO5]	[10M]
10	Explain the concept of Discontinuous Space Vector Modulation.	[L4][CO5]	[10M]

UNIT -V MULTILEVEL INVERTERS

1	Explain the working principle of Cascaded H-Bridge (CHB) multilevel inverter with equal DC voltage sources.	[L2][CO6]	[10M]
2	Discuss Cascaded H-Bridge multilevel inverter with unequal DC voltage sources.	[L2][CO6]	[10M]

3	Explain Phase-Shifted Multicarrier Modulation for multilevel inverters.	[L3][CO6]	[10M]
4	Explain level-Shifted Multicarrier Modulation for multilevel inverters.	[L2][CO6]	[10M]
5	Explain Staircase Modulation in Cascaded H-Bridge (CHB) multilevel inverter	[L2][CO6]	[10M]
6	Explain the commutation of switching devices in the three level NPC inverter.	[L2][CO6]	[10M]
7	Explain space vector modulation (SVM) scheme for the three-level NPC inverter with dwell time calculations.	[L2][CO6]	[10M]
8	Explain the Effect of Switching States on Neutral-Point Voltage Deviation in three-level NPC inverter	[L2][CO6]	[10M]
9	Explain the Switching Sequence with Minimal Neutral-Point Voltage Deviation in three-level NPC inverter.	[L2][CO6]	[10M]
10	Explain the concept of Even-Order Harmonic Elimination in three-level NPC inverter.	[L2][CO6]	[10M]

PREPARED BY: Dr G.Muni Reddy
Professor
Dept. of EEE
SIETK, PUTTUR